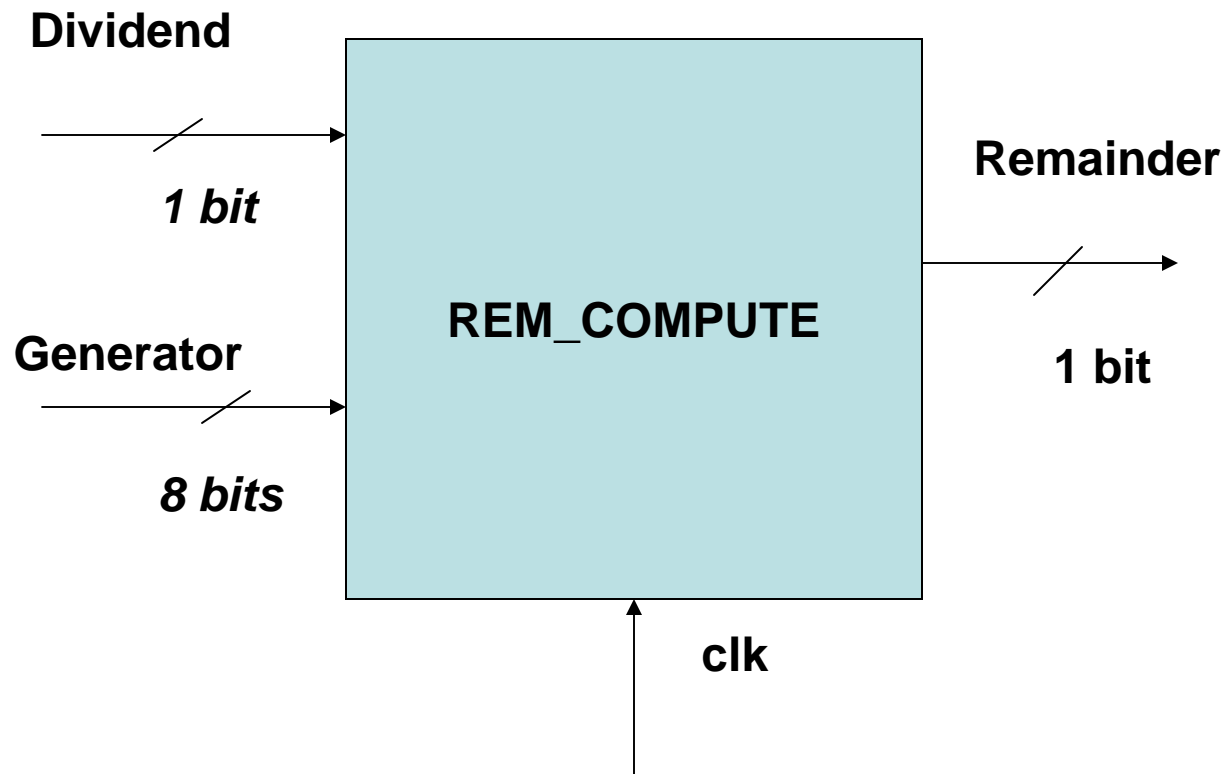


# First Project Assignment

# Verify the following circuit using Specman Elite

**Design:** The circuit computes the remainder for ECC CRC-8 with generator  $x^8+x^2+x+1$ . The remainder from the generator is a polynomial of degree, at most seven and thus can be encoded as a byte, whose bits are the remainder's coefficient.

# Block Diagram



$$\text{Generator} = x^8 + x^2 + x + 1 = (100000111)_2$$

$$\begin{aligned} \text{Input Polynomial} &= x^{14} + x^{13} + x^{11} + x^9 + x^7 + x^5 + x^2 + 1 \\ &= (110101010100101)_2. \end{aligned}$$

# An Example

$$\begin{array}{r}
 \begin{array}{r}
 1101011 \leftarrow \text{QUOTIENT} \\
 \hline
 100000111 \overline{) 110101010100101} \\
 \phantom{100000111} \uparrow \\
 \phantom{100000111} 100000111 \\
 \phantom{100000111} \text{Generator} \quad \text{-----} \\
 \phantom{100000111} \phantom{100000111} \\
 \phantom{100000111} \phantom{100000111} 101011011 \\
 \phantom{100000111} \phantom{100000111} 100000111 \\
 \phantom{100000111} \phantom{100000111} \text{-----} \\
 \phantom{100000111} \phantom{100000111} 101110000 \\
 \phantom{100000111} \phantom{100000111} 100000111 \\
 \phantom{100000111} \phantom{100000111} \text{-----} \\
 \phantom{100000111} \phantom{100000111} 111011110 \\
 \phantom{100000111} \phantom{100000111} 100000111 \\
 \phantom{100000111} \phantom{100000111} \text{-----} \\
 \phantom{100000111} \phantom{100000111} 110110011 \\
 \phantom{100000111} \phantom{100000111} 100000111 \\
 \phantom{100000111} \phantom{100000111} \text{-----} \\
 \phantom{100000111} \phantom{100000111} 10110100 \leftarrow \text{REMAINDER}
 \end{array}
 \end{array}$$

# A Basic Circuit

